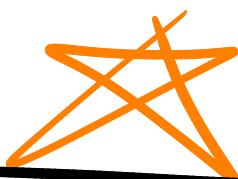


CMPT 476 Lecture 2

... The circuit model...




Last class we learned that quantum computation is **linear** (i.e. matrices & vectors). Today we'll build a **linear algebraic** model of **Classical Computing** which will extend nicely to **probabilistic** and then **quantum** computing.

(The circuit model)

Circuit models are simple (**but powerful**) models of computation based around **composition** of a set of basic operations called **gates**.

Wires are used to connect inputs & outputs of gates. We draw circuits **graphically** as below

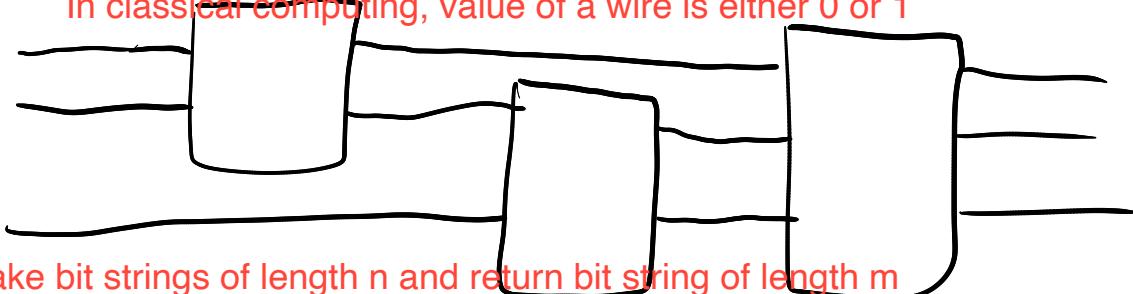In classical computing, value of a wire is either 0 or 1



Operations take bit strings of length n and return bit string of length m

What is the significance of two states being correlated?



time

(Classical circuits)

In the classical circuit model...

- The state of a bit/wire is 0 or 1
- The state of n bits is a bitstring

$$x \in \{0,1\}^n$$

- Computations are functions

$$f: \{0,1\}^n \rightarrow \{0,1\}^m$$

As a gate,


$$n \text{ inputs } \{ \underset{\square}{f} \} m \text{ outputs}$$

Ex.

The NOT gate is a 1-bit function which computes the Boolean not (\neg): $\text{NOT}(x) = \neg x$. We can write the function explicitly via a truth table.


Input	X	NOT(x)	Output
0		1	
1		0	

We draw a NOT gate as

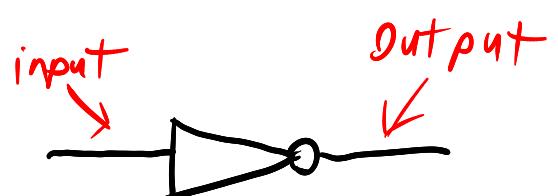


Ex.


Other common gates are:

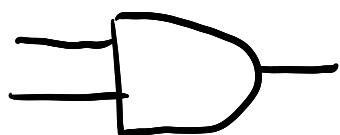

$$AND(x, y) = x \wedge y$$

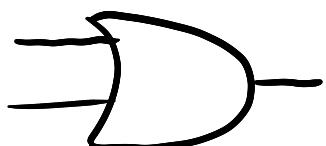

$$OR(x, y) = x \vee y$$

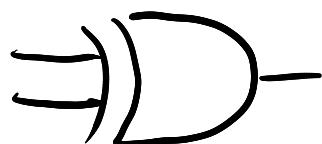


$$XOR(x, y) = x \oplus y$$

Their truth tables are

x	y	AND(x, y)	OR(x, y)	XOR(x, y)
0	0	0	0	0
0	1	0	1	1
1	0	0	1	1
1	1	1	1	0

Ex.

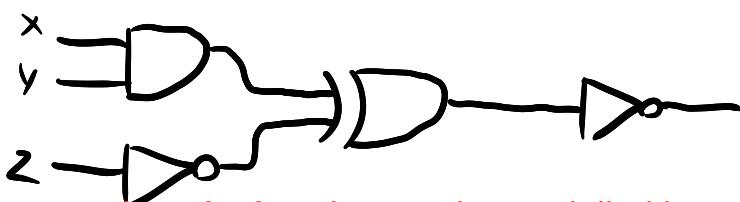What function does this circuit implement?



Computation of a function can be modelled by a series of gates

We list out each intermediate value in the truth table:

x	y	z	a = AND(x, y)	b = NOT(z)	c = XOR(a, b)	NOT(c)
0	0	0	0	1	1	0
0	0	1	0	0	0	1
0	1	0	0	1	1	0
0	1	1	0	0	0	1
1	0	0	0	1	1	0
1	0	1	0	0	0	1
1	1	0	1	1	0	1
1	1	1	1	0	1	0

(Universality)

A set of gates Γ is **universal for classical computation** if for any $n, m > 0$ and $f: \{0, 1\}^n \rightarrow \{0, 1\}^m$, a circuit computing f can be constructed using only gates in Γ .

(FANOUT)

In classical computing we often assume we can use a bit any number of times in a computation. Formally, this is achieved through the **FANOUT** or **copy** gate



elements, do we assume that using fanout on a bit automatically renders that bit null?

Thm.

How can you make a copy without measuring the state?

The set $\{\text{AND}, \text{XOR}, \text{NOT}, \text{FANOUT}\}$ is universal.
XOR gate is preferred over OR gate.
why?


(Translating between gate sets)

We can **translate** circuits written in one gate set to another by replacing each gate with an equivalent circuit.

E.X.



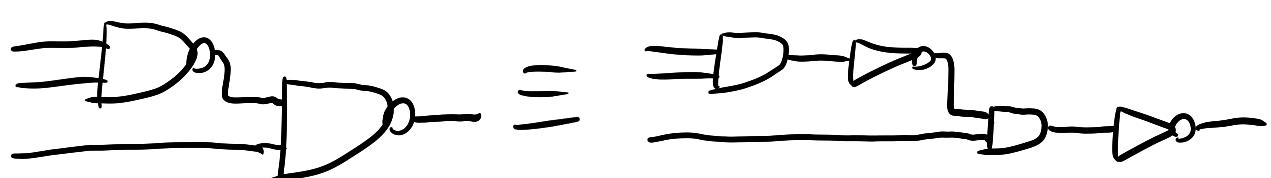translate NAND gates to a composition of AND and NOT gates




(Probabilistic circuits)

(hence quantum)

What if we wanted to model probabilistic computation?
We could say a bit with probability $p \in [0, 1]$
of being "1" has state p . Does this work?

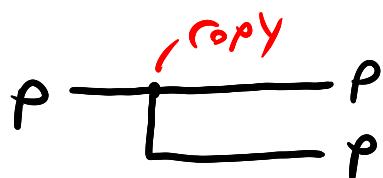You talk about
the complexity
of a circuit with
respect to a
gate set.



The final state above has probabilities

$$00 \rightarrow (1-p)(1-p)$$

$$01 \rightarrow (1-p)p$$

Is there destructive interference that gets rid of the 10 and 01 states?

$$10 \rightarrow p(1-p)$$

Since fanout only makes a copy of a bit, it should not give us states with differing bits

$$11 \rightarrow p^2$$

To represent probabilistic computations, we need to change the way that we think

BUT the states 01 and 10 are impossible!

The problem here is we can't express joint probability distributions. For this we need more degrees of freedom in our state description!

(Linear algebraic circuits)

In the linear algebraic view, we can represent a bit with probability p in the 1 state as

$$\begin{bmatrix} 1-p \\ p \end{bmatrix}$$

If $p=0$, then we have state $\begin{bmatrix} 1 \\ 0 \end{bmatrix}$, or 0, and if $p=1$, then we have state $\begin{bmatrix} 0 \\ 1 \end{bmatrix}$ or 1.

Equivalently, we can describe the state as

$$(1-p)\begin{bmatrix} 1 \\ 0 \end{bmatrix} + p\begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

(Linear algebraic gates)

Suppose we apply NOT to the probabilistic state $\begin{bmatrix} p_1 \\ p_0 \end{bmatrix}$. Then we have probability p_1 of being 1 and p_0 of being 0, or $\begin{bmatrix} p_0 \\ p_1 \end{bmatrix}$. This transformation can be described as a transition matrix $\begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$.

$$\begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} p_1 \\ p_0 \end{bmatrix} = \begin{bmatrix} p_0 \\ p_1 \end{bmatrix}$$

Note also that

$$\begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}, \quad \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

So NOT $\equiv \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$ sends 0 to 1 and vice versa

(Multiple bits)

Given two bits $\begin{bmatrix} p_1 \\ p_0 \end{bmatrix}$ and $\begin{bmatrix} q_1 \\ q_0 \end{bmatrix}$ we can write their joint probability distribution as

$$\begin{bmatrix} p_1 q_1 \\ p_1 q_0 \\ p_0 q_1 \\ p_0 q_0 \end{bmatrix} \leftarrow \begin{array}{l} 00 \\ 01 \\ 10 \\ 11 \end{array}$$

This is called the tensor product

$$\begin{bmatrix} p_1 \\ p_0 \end{bmatrix} \otimes \begin{bmatrix} q_1 \\ q_0 \end{bmatrix} = \begin{bmatrix} p_1 [q_1] \\ p_1 [q_0] \\ p_0 [q_1] \\ p_0 [q_0] \end{bmatrix} = \begin{bmatrix} p_1 q_1 \\ p_1 q_0 \\ p_0 q_1 \\ p_0 q_0 \end{bmatrix}$$

(Correlated Distributions)

A distribution $\begin{bmatrix} a \\ b \\ c \\ d \end{bmatrix}$ is **correlated** if it can't be written as a tensor product $\begin{bmatrix} a \\ b \\ c \\ d \end{bmatrix} = \begin{bmatrix} a_1 \\ b_1 \\ c_1 \\ d_1 \end{bmatrix} \otimes \begin{bmatrix} a_2 \\ b_2 \\ c_2 \\ d_2 \end{bmatrix}$. Otherwise we say it is **Separable**.

Ex.

The CNOT or controlled-NOT gate takes 2 bits and applies NOT to the second if and only if the first is 1. As a matrix,

10: first coin in tail state, second coin in head state

$$\begin{array}{l}
 \text{Input} \rightarrow \begin{matrix} 00 & 01 & 10 & 11 \end{matrix} \\
 \begin{matrix} 0: \text{head state} \\ 1: \text{tail state} \end{matrix} \quad \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix} \quad \begin{matrix} 00 \\ 01 \\ 10 \\ 11 \end{matrix} \leftarrow \text{Output}
 \end{array}$$

0 state

Applying CNOT to the state $\begin{bmatrix} 0.25 \\ 0.75 \end{bmatrix} \otimes \begin{bmatrix} 1 \\ 0 \end{bmatrix}$ gives

information about the first bit since the transformation only occurs if it is in the 1 state.

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} 0.25 \\ 0 \\ 0.75 \\ 0 \end{bmatrix} = \begin{bmatrix} 0.25 \\ 0 \\ 0 \\ 0.75 \end{bmatrix} \quad \begin{matrix} 00 \\ 01 \\ 10 \\ 11 \end{matrix}$$

Now suppose

$$\begin{bmatrix} 0.25 \\ 0 \\ 0 \\ 0.75 \end{bmatrix} = \begin{bmatrix} a \\ b \\ c \\ d \end{bmatrix} \otimes \begin{bmatrix} e \\ f \end{bmatrix} = \begin{bmatrix} ae \\ be \\ ce \\ de \end{bmatrix}$$

Quantum context: correlated = entangled

Then $ae = 0.25$, $ad = 0 \Rightarrow d = 0$, but then $bd = 0$, a contradiction, so the distribution is **correlated**.

(A note on vectors & matrices)

We used the term **distribution** informally. Formally, a vector (i.e. state) $p \in \mathbb{R}^n$ (real vector space of $\dim n$) is a distribution on $\{0, \dots, n-1\}$ or simply a **probability vector** if

1. $p_i \geq 0$ for all i

2. $\sum_i p_i = 1$ Note: this is the 1-norm

If States are probability vectors, then gates should map distributions to distributions. These are exactly the **stochastic** matrices A , which have as columns A_i probability vectors.

Ex.

$A = \begin{bmatrix} \frac{1}{2} & \frac{1}{2} \\ \frac{1}{2} & \frac{1}{2} \end{bmatrix}$ is a stochastic matrix modeling a **coin flip**. Calling $\begin{bmatrix} 1 \\ 0 \end{bmatrix}$ **heads** and $\begin{bmatrix} 0 \\ 1 \end{bmatrix}$ **tails**, we have

$$A \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \begin{bmatrix} \frac{1}{2} \\ \frac{1}{2} \end{bmatrix} = \frac{1}{2} \begin{bmatrix} 1 \\ 0 \end{bmatrix} + \frac{1}{2} \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$A \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \frac{1}{2} \begin{bmatrix} 1 \\ 0 \end{bmatrix} + \frac{1}{2} \begin{bmatrix} 0 \\ 1 \end{bmatrix} = \begin{bmatrix} \frac{1}{2} \\ \frac{1}{2} \end{bmatrix}$$

the input state is irrelevant!

In quantum computing, our allowable operations will take on a very similar restriction 😊

What is universality?

It is the circuit model?